Light dependent resistor (LDR)

Low output when dark
High output when light

+5V

LDR

OUT

R1 5k ... 10k

GND

High output when dark
Low output when light

+5V

R2 5k ... 10k

OUT

LDR1

GND

LDR configurations

LDR

not saved!

Simon de Bakker

Sheet: 1/1

Rev:1.0